


ELECTRÓNICA BÁSICA

Amplificadores Diferenciales Problemas

ResPrB.IV-1

Problema 1(a)

- Análisis en dc:

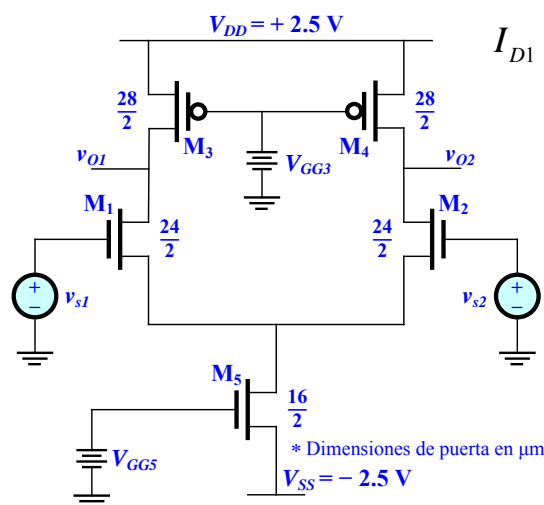

$$I_{D1} = 50 \mu\text{A} \rightarrow I_{D5} = 100 \mu\text{A}$$

$$V_{GS5} = V_{TON} + \sqrt{\frac{2L_5 I_{D5}}{W_5 K'_n}} = 1.27 \text{ V}$$


$$V_{GG5} = V_{GS5} + V_{SS} = -1.23 \text{ V}$$

* Dimensiones de puerta en μm
 $V_{SS} = -2.5 \text{ V}$

ResPrB.IV-2

Problema 1(a)

- Análisis en ac:

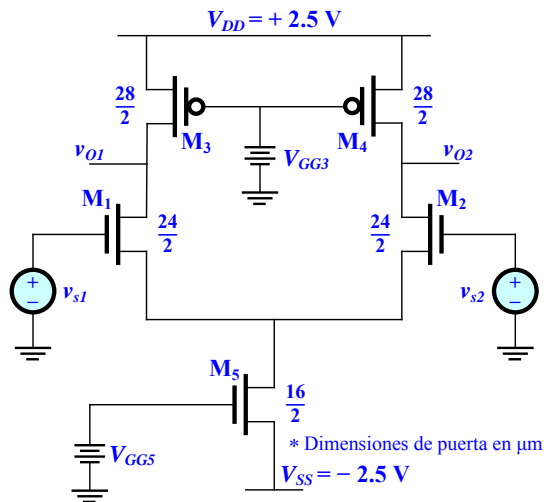

$$I_{DP3} = I_{D1} = 50 \mu\text{A}$$

$$I_{DP4} = I_{D2} = 50 \mu\text{A}$$

$$I_{D5} = 100 \mu\text{A}$$

$$g_{m1} = 366.6 \mu\text{A/V}$$

$$g_{ds1} = 0.5 \mu\text{A/V}$$

$$g_{ds3} = 1 \mu\text{A/V}$$

$$g_{ds5} = 1 \mu\text{A/V}$$

ResPrB.IV-3

Problema 1(a)

- Análisis en ac:

$$A_{dm} = -\frac{g_{m1}}{g_{ds1} + g_{ds3}} = -244.4$$

$$A_{cm} = -\frac{g_{m1}}{g_{ds1} + g_{ds3} + \frac{2g_{ds3}(g_{m1} + g_{ds1})}{g_{ds5}}} = -0.5$$

$$v_{o1} = A_{dm}(v_{s1} - v_{s2})/2 + A_{cm}(v_{s1} + v_{s2})/2$$

$$v_{o2} = -A_{dm}(v_{s1} - v_{s2})/2 + A_{cm}(v_{s1} + v_{s2})/2$$


$$v_{o1} = -122.2(v_{s1} - v_{s2}) - 0.25(v_{s1} + v_{s2})$$

$$v_{o2} = 122.2(v_{s1} - v_{s2}) - 0.25(v_{s1} + v_{s2})$$

ResPrB.IV-4

Problema 1(b)

- Análisis en dc:

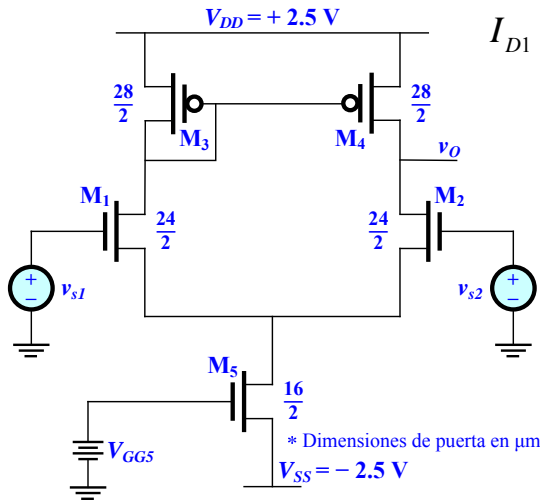

$$I_{D1} = 50 \mu\text{A} \rightarrow I_{D5} = 100 \mu\text{A}$$


$$V_{GS5} = V_{TON} + \sqrt{\frac{2L_5 I_{D5}}{W_5 K'_n}} = 1.27 \text{ V}$$

$$V_{GG5} = V_{GS5} + V_{SS} = -1.23 \text{ V}$$

ResPrB.IV-5

Problema 1(b)

- Análisis en ac:

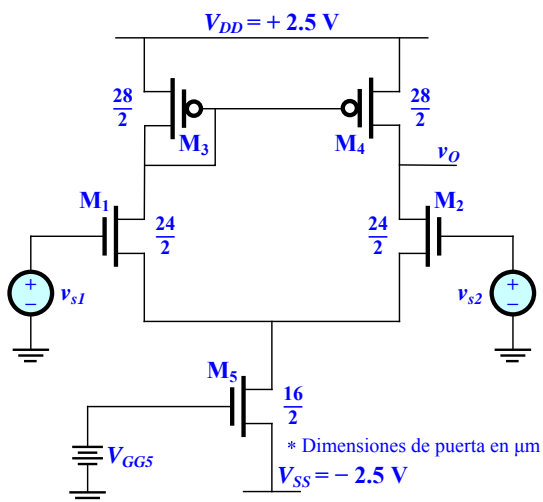

$$I_{DP3} = I_{D1} = 50 \mu\text{A}$$

$$I_{DP4} = I_{D2} = 50 \mu\text{A}$$

$$I_{D5} = 100 \mu\text{A}$$

$$g_{m2} = 366.6 \mu\text{A/V}$$

$$g_{ds2} = 0.5 \mu\text{A/V}$$

$$g_{m4} = 245.3 \mu\text{A/V}$$

$$g_{ds4} = 1 \mu\text{A/V}$$

$$g_{ds5} = 1 \mu\text{A/V}$$

ResPrB.IV-6

Problema 1(b)

- Análisis en ac:

$$A_{dm} = \frac{g_{m2}}{g_{ds2} + g_{ds4}} = 244.4$$


$$A_{cm} = \frac{-g_{ds5}g_{ds2}}{2g_{m4}(g_{ds2} + g_{ds4})} = -0.68 \cdot 10^{-3}$$

$$\begin{aligned} v_{out} &= A_{dm}(v_{i1} - v_{i2}) + A_{cm} \frac{(v_{i1} + v_{i2})}{2} = \\ &= 244.4 \cdot (v_{i1} - v_{i2}) - 0.34 \cdot 10^{-3} \cdot (v_{i1} + v_{i2}) \end{aligned}$$

ResPrB.IV-7

Problema 2

- Amplificador CMOS fuente común:

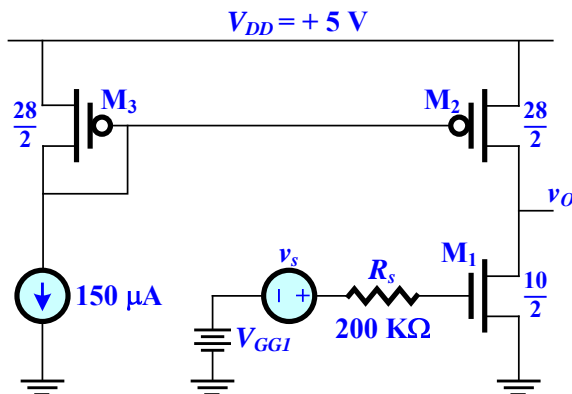


C_{gs1}	25 fF
C_{gd1}	2 fF
C_{gb1}	0.2 fF
C_{db1}	13 fF
C_{gd2}	5.6 fF
C_{ab2}	34.2 fF

ResPrB.IV-8

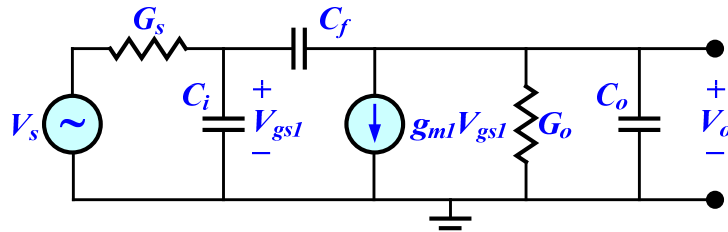Problema 2

- Circuito de pequeña señal en alta frecuencia:



$$g_{m1} = 409.8 \mu\text{A/V} \quad , \quad R_s = 200 \text{ K}\Omega$$

$$G_o = g_{ds1} + g_{ds2} = 4.5 \mu\text{A/V} \quad \rightarrow \quad R_o = 222 \text{ K}\Omega$$


$$C_i = C_{gs1} + C_{gb1} = 25.2 \text{ fF} \quad , \quad C_f = C_{gd1} = 2 \text{ fF}$$

$$C_o = C_{gd2} + C_{db1} + C_{db2} = 52.8 \text{ fF}$$

ResPrB.IV-9

Problema 2

- Ganancia de tensión:

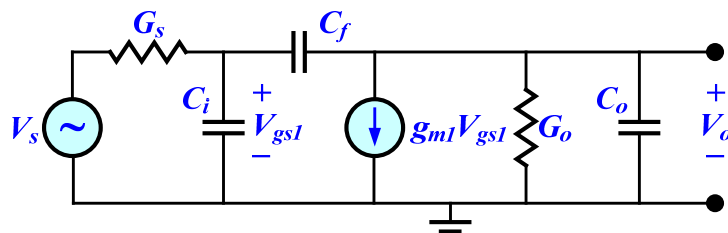

$$\frac{V_o(s)}{V_s(s)} = \frac{R_o (sC_f - g_{m1})}{b_2 s^2 + b_1 s + 1}$$

$$b_2 = R_s R_o (C_i C_o + C_i C_f + C_o C_f)$$

$$b_1 = R_s (1 + g_{m1} R_o) C_f + R_s C_i + R_o (C_o + C_f)$$

ResPrB.IV-10

Problema 2

- Modelo completo:

$$\frac{V_o(s)}{V_s(s)} = \frac{R_o(sC_f - g_{m1})}{b_2s^2 + b_1s + 1}$$

$$z_1 = 204.9 \times 10^9 \text{ rad/seg}$$

$$p_2 = -799 \times 10^6 \text{ rad/seg}$$

$$p_1 = -18.9 \times 10^6 \text{ rad/seg}$$

$$w_c = 18.95 \times 10^6 \text{ rad/seg} \rightarrow f_c = 3 \text{ MHz}$$

ResPrB.IV-11

Problema 2

- Aproximación de polo dominante:

$$p_1 \approx -\frac{1}{R_s(1 + g_{m1}R_o)C_f + R_sC_i + R_o(C_o + C_f)}$$

$$p_2 \approx -\frac{R_s(1 + g_{m1}R_o)C_f + R_sC_i + R_o(C_o + C_f)}{R_sR_o(C_iC_o + C_iC_f + C_oC_f)}$$


$$p_1 \approx -18.5 \times 10^6 \text{ rad/seg} \rightarrow f_c = 2.9 \text{ MHz}$$

$$p_2 \approx -818 \times 10^6 \text{ rad/seg}$$

ResPrB.IV-12

Problema 2

- Aproximación Miller:

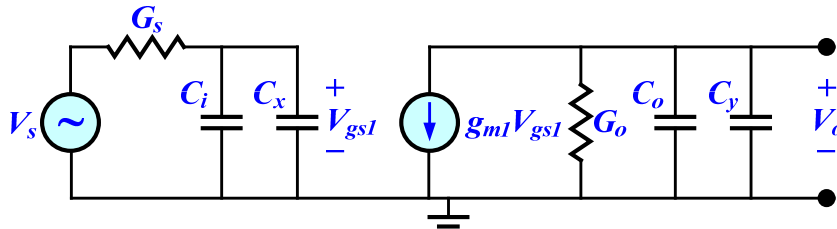

$$A_{v0} = \frac{v_o}{v_{gs1}} = -g_{m1}R_o = -90.9$$


$$C_x \approx (1 - A_{v0})C_f = (1 + g_{m1}R_o)C_f = 183.9 \text{ fF}$$

$$C_y \approx \left(1 - \frac{1}{A_{v0}}\right)C_f = \left(1 + \frac{1}{g_{m1}R_o}\right)C_f = 2 \text{ fF}$$

ResPrB.IV-13

Problema 2

- Aproximación Miller:

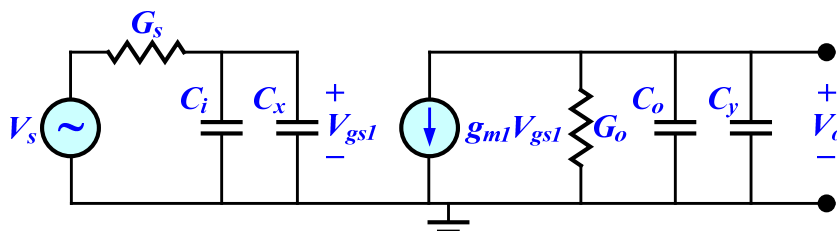


$$\frac{V_o(s)}{V_s(s)} = \frac{-g_{m1}R_o}{(1 + R_s(C_i + C_x)s)(1 + R_o(C_o + C_y)s)}$$

ResPrB.IV-14

Problema 2

- Aproximación Miller:

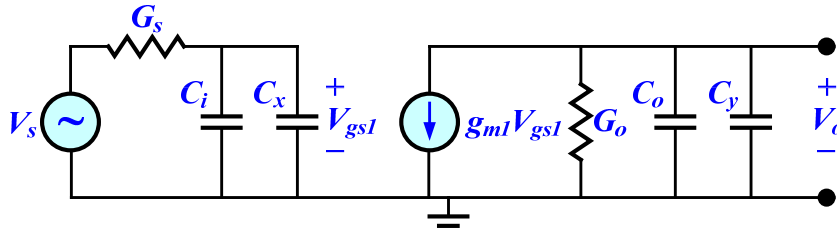

$$p_1 = -\left(R_s C_i + R_s (1 + g_{m1} R_o) C_f\right)^{-1} = -23.9 \times 10^6 \text{ rad/seg}$$


$$p_2 = -\left(R_o C_o + R_o \left(1 + (g_{m1} R_o)^{-1}\right) C_f\right)^{-1} = -82.1 \times 10^6 \text{ rad/seg}$$

$$f_c \approx \left(2\pi \left(R_s C_i + R_s (1 + g_{m1} R_o) C_f\right)\right)^{-1} = 3.8 \text{ MHz}$$

ResPrB.IV-15

Problema 3

- Análisis en dc:

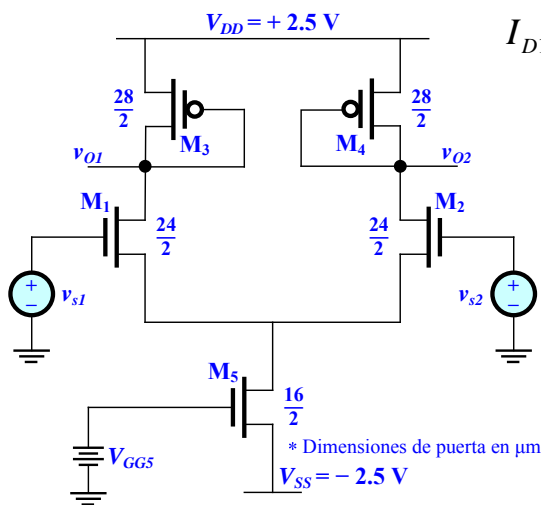

$$I_{D1} = 50 \mu\text{A} \rightarrow I_{D5} = 100 \mu\text{A}$$


$$V_{GS5} = V_{TON} + \sqrt{\frac{2L_5 I_{D5}}{W_5 K_n}} = 1.27 \text{ V}$$

$$V_{GG5} = V_{GS5} + V_{SS} = -1.23 \text{ V}$$

ResPrB.IV-16

Problema 3

- Análisis en dc:

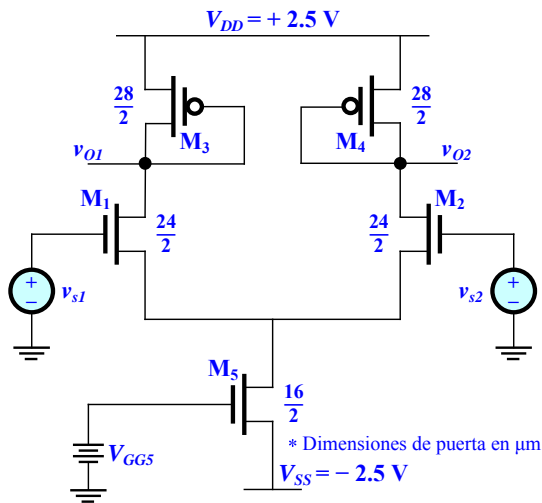

$$V_{GS1} = V_{GS2} =$$

$$= V_{TON} + \sqrt{\frac{2L_2 I_{D2}}{W_2 K'_n}} =$$

$$= 1.07 \text{ V}$$

$$V_{SG3} = V_{SG4} =$$


$$= |V_{TOP}| + \sqrt{\frac{2L_4 I_{DP4}}{W_4 K'_p}}$$

$$= 1.3 \text{ V}$$

ResPrB.IV-17

Problema 3

- Análisis en ac:

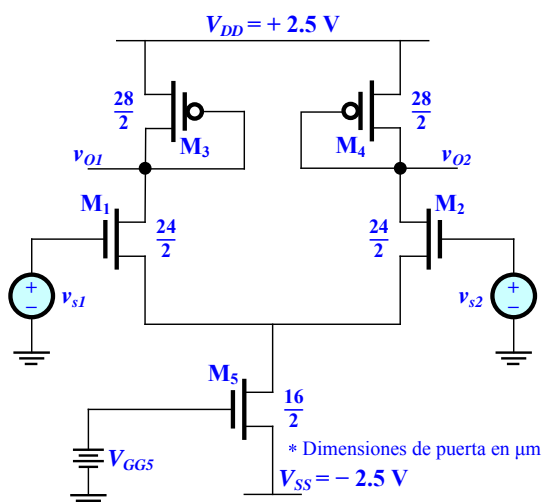

$$I_{DP3} = I_{D1} = 50 \mu\text{A}$$

$$I_{DP4} = I_{D2} = 50 \mu\text{A}$$

$$I_{D5} = 100 \mu\text{A}$$

$$g_{m1} = 366.6 \mu\text{A/V}$$

$$g_{ds1} = 0.5 \mu\text{A/V}$$

$$g_{m3} = 245.3 \mu\text{A/V}$$

$$g_{ds3} = 1 \mu\text{A/V}$$

$$g_{ds5} = 1 \mu\text{A/V}$$

ResPrB.IV-18

Problema 3

- Análisis en ac:

$$A_{dm} = -\frac{g_{m1}}{g_{ds1} + g_{m3} + g_{ds3}} = -1.48$$

$$A_{cm} = -\frac{g_{m1}}{g_{ds1} + g_{m3} + g_{ds3} + \frac{2(g_{m3} + g_{ds3})(g_{m1} + g_{ds1})}{g_{ds5}}} = -2 \cdot 10^{-3}$$

$$v_{o1} = -0.74(v_{s1} - v_{s2}) - (v_{s1} + v_{s2}) \cdot 10^{-3}$$

$$v_{o2} = 0.74(v_{s1} - v_{s2}) - (v_{s1} + v_{s2}) \cdot 10^{-3}$$

ResPrB.IV-19