
ELECTRÓNICA BÁSICA


El Transistor MOS Problemas

ResPrB.I-1

Problema 1(a)

- M_1 EOSat:

$$V_{GS1} - V_{TON} = V_{DS1}$$

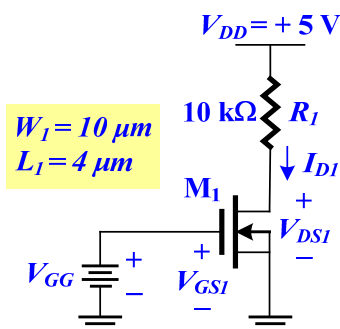

$$\begin{aligned} I_{D1} &= \frac{1}{2} \frac{W_1}{L_1} K'_n (V_{GS1} - V_{TON})^2 \\ &= \frac{1}{2} \frac{W_1}{L_1} K'_n V_{DS1}^2 \\ &= \frac{V_{DD} - V_{DS1}}{R_1} \end{aligned}$$


$$V_{DS1}^2 + \frac{5}{7} V_{DS1} - \frac{25}{7} = 0 \rightarrow V_{DS1} = 1.566 V$$

$$V_{GG} = V_{GS1} = V_{DS1} + V_{TON} = 2.366 V, \quad I_{D1} = \frac{V_{DD} - V_{DS1}}{R_1} = 343 \mu A$$

ResPrB.I-2

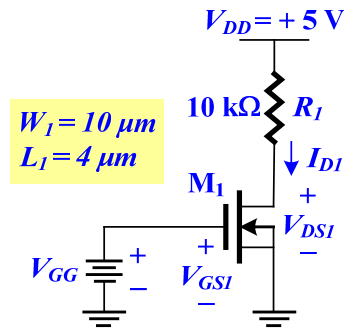Problema 1(a)

- $V_{GG} = 1\text{ V}$, $V_{GS1} = 1\text{ V}$, $M_1 \equiv \text{SAT}$:



$$I_{D1} = \frac{1}{2} \frac{W_1}{L_1} K'_n (V_{GS1} - V_{TON})^2$$

$$= 5.6 \mu\text{A}$$

$$V_{DS1} = V_{DD} - I_{D1} R_1 = 4.944\text{ V}$$


Test de saturación:

$$V_{GS1} - V_{TON} = 0.2\text{ V} < V_{DS1} = 4.944\text{ V}$$

ResPrB.I-3

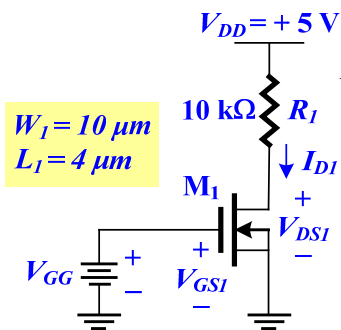Problema 1(a)

- $V_{GG} = 2.5\text{ V}$, $V_{GS1} = 2.5\text{ V}$, $M_1 \equiv \text{Lin}$:



$$I_{D1} = \frac{W_1}{L_1} K'_n \left((V_{GS1} - V_{TON}) V_{DS1} - \frac{1}{2} V_{DS1}^2 \right)$$

$$= \frac{V_{DD} - V_{DS1}}{R_1}$$

$$V_{DS1}^2 - \left(\frac{5}{7} + 3.4 \right) V_{DS1} + \frac{25}{7} = 0$$


$$\rightarrow V_{DS1} = 1.244\text{ V} \rightarrow I_{D1} = 375.6 \mu\text{A}$$

Test de zona lineal: $V_{GS1} - V_{TON} = 1.7\text{ V} > V_{DS1} = 1.244\text{ V}$

ResPrB.I-4

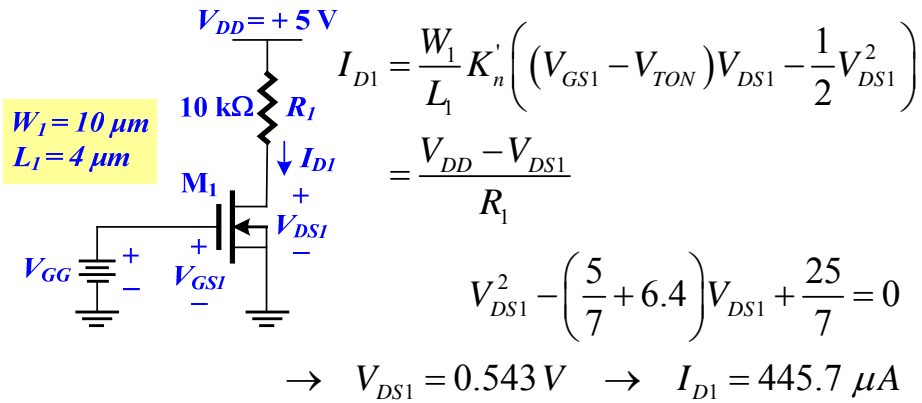Problema 1(a)

- $V_{GG} = 4V$, $V_{GS1} = 4V$, $M_1 \equiv \text{Lin}$:




Test de zona lineal: $V_{GS1} - V_{TON} = 3.2V > V_{DS1} = 0.543V$

ResPrB.I-5

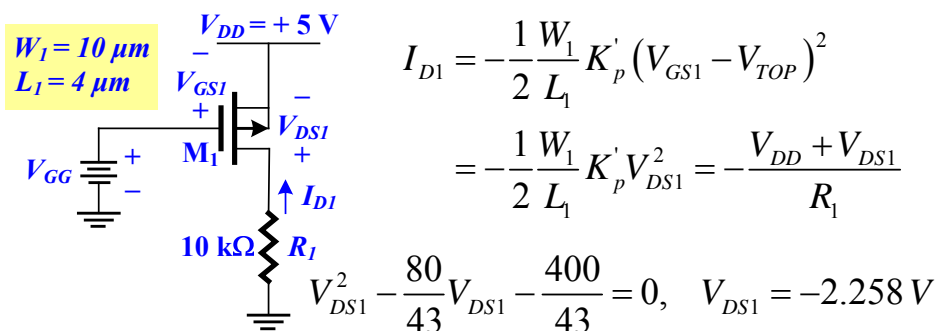Problema 1(b)

- M_1 EOSat: $V_{GS1} - V_{TOP} = V_{DS1}$




$V_{GS1} = V_{DS1} + V_{TOP} = -3.158V$, $V_{GG} = V_{DD} + V_{GS1} = 1.842V$

$I_{D1} = -\frac{V_{DD} + V_{DS1}}{R_1} = -274 \mu A$, $I_{DP1} = -I_{D1} = 274 \mu A$

ResPrB.I-6

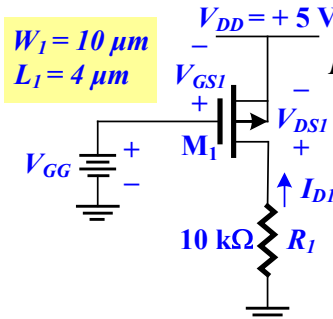Problema 1(b)

- $V_{GG} = 1V$, $V_{GS1} = -4V$, $M_1 \equiv LIN$:



$$I_{D1} = -\frac{W_1}{L_1} K'_p \left((V_{GS1} - V_{TOP}) V_{DS1} - \frac{1}{2} V_{DS1}^2 \right)$$

$$= -\frac{V_{DD} + V_{DS1}}{R_1}$$

$$V_{DS1}^2 + \left(6.2 + \frac{80}{43} \right) V_{DS1} + \frac{400}{43} = 0$$


$$\rightarrow V_{DS1} = -1.395V \quad , \quad I_{D1} = -360.5 \mu A$$

Test de zona lineal: $V_{GS1} - V_{TOP} = -3.1 < V_{DS1} = -1.395$

ResPrB.I-7

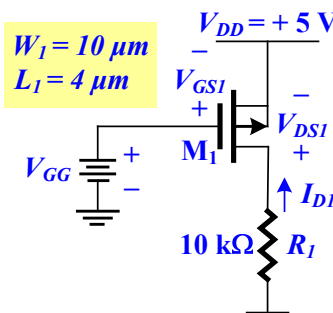Problema 1(b)

- $V_{GG} = 2.5V$, $V_{GS1} = -2.5V$, $M_1 \equiv SAT$:



$$I_{D1} = -\frac{1}{2} \frac{W_1}{L_1} K'_p (V_{GS1} - V_{TOP})^2$$

$$= -\frac{V_{DD} + V_{DS1}}{R_1}$$

$$\frac{430}{8} 2.56 = 500 + 100V_{DS1}$$


$$\rightarrow V_{DS1} = -3.624V \quad , \quad I_{D1} = -137.6 \mu A$$

Test de saturacion: $V_{GS1} - V_{TOP} = -1.6V > V_{DS1} = -3.624V$

ResPrB.I-8

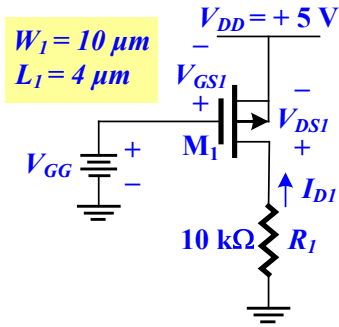Problema 1(b)

- $V_{GG} = 4\text{ V}$, $V_{GS1} = -1\text{ V}$, $M_1 \equiv \text{SAT}$:



$$I_{D1} = -\frac{1}{2} \frac{W_1}{L_1} K'_p (V_{GS1} - V_{TOP})^2$$

$$= -\frac{V_{DD} + V_{DS1}}{R_1}$$

$$\frac{430}{8} 0.01 = 500 + 100V_{DS1}$$


$$\rightarrow V_{DS1} = -4.994\text{ V}, \quad I_{D1} = -0.54\ \mu\text{A}$$

Test de saturación: $V_{GS1} - V_{TOP} = -0.1\text{ V} > V_{DS1} = -4.994\text{ V}$

ResPrB.I-9

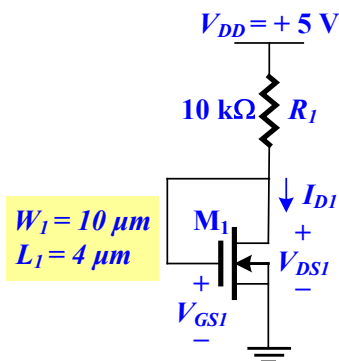Problema 2(a)

- $V_{GS1} = V_{DS1} \rightarrow M_1 \equiv \text{SAT}$



$$I_{D1} = \frac{1}{2} \frac{W_1}{L_1} K'_n (V_{GS1} - V_{TON})^2$$

$$= \frac{V_{DD} - V_{GS1}}{R_1}$$

$$V_{GS1}^2 - \left(1.6 - \frac{5}{7}\right) V_{GS1} + 0.64 - \frac{25}{7} = 0$$


$$\rightarrow V_{GS1} = V_{DS1} = 2.21\text{ V}$$

$$\rightarrow I_{D1} = \frac{V_{DD} - V_{DS1}}{R_1} = 279\ \mu\text{A}$$

ResPrB.I-10

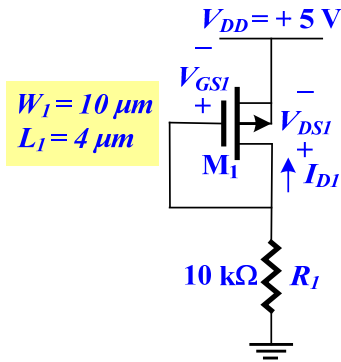Problema 2(b)

- $V_{GS1} = V_{DS1} \rightarrow M_1 \equiv SAT$



$$I_{D1} = -\frac{1}{2} \frac{W_1}{L_1} K'_p (V_{GS1} - V_{TOP})^2$$

$$= -\frac{V_{DD} + V_{GS1}}{R_1}$$

$$V_{GS1}^2 + \left(1.8 - \frac{80}{43}\right) V_{GS1} + 0.81 - \frac{400}{43} = 0$$

$$\rightarrow V_{GS1} = V_{DS1} = -2.884 \text{ V}$$


$$\rightarrow I_{D1} = \frac{-V_{DD} - V_{DS1}}{R_1} = -211.6 \mu\text{A}$$

ResPrB.I-11

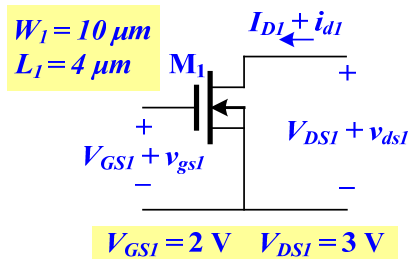Problema 3(a)

- $M_1 \equiv SAT : V_{GS1} - V_{TON} = 1.2 \text{ V} < V_{DS1} = 3 \text{ V}$

$$I_{D1} = \frac{1}{2} \frac{W_1}{L_1} K'_n (V_{GS1} - V_{TON})^2 (1 + \lambda_n V_{DS}) = 204 \mu\text{A}$$



$$g_m = \sqrt{2 \frac{W}{L} K'_n I_{D1} (1 + \lambda_n V_{DS1})}$$

$$= 340 \mu\text{A/V}$$


$$g_{ds} = \frac{\lambda_n I_{D1}}{(1 + \lambda_n V_{DS1})} = 0.806 \mu\text{A/V}$$

$$r_{ds} = g_{ds}^{-1} = 1.24 \text{ M}\Omega$$

ResPrB.I-12

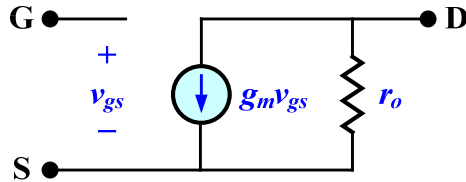Problema 3(a)

- Circuito equivalente de pequeña señal en LF:




$$g_m = 340 \mu\text{A/V} \quad r_o = 1.24 \text{M}\Omega$$

ResPrB.I-13

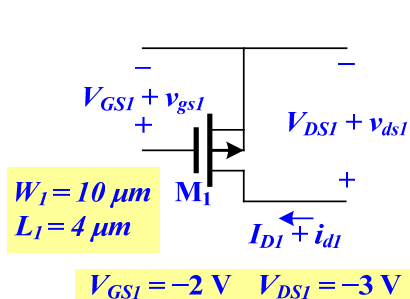Problema 3(b)

- $M_1 \equiv \text{SAT} : V_{GS1} - V_{TOP} = -1.1 \text{V} > V_{DS1} = -3 \text{V}$

$$I_{D1} = -\frac{1}{2} \frac{W_1}{L_1} K'_p (V_{GS1} - V_{TOP})^2 (1 - \lambda_p V_{DS}) = -66.4 \mu\text{A}$$



$$g_m = \sqrt{2 \frac{W}{L} K'_p |I_{D1}| (1 - \lambda_p V_{DS1})}$$

$$= 120.7 \mu\text{A/V}$$


$$g_{ds} = \frac{\lambda_p |I_{D1}|}{(1 - \lambda_p V_{DS1})} = 0.455 \mu\text{A/V}$$

$$r_{ds} = g_{ds}^{-1} = 2.2 \text{M}\Omega$$

ResPrB.I-14

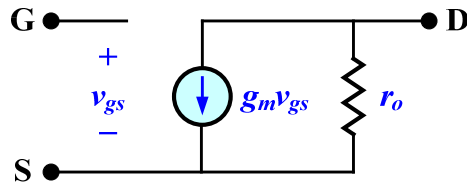Problema 3(b)

- Circuito equivalente de pequeña señal en LF:




$$g_m = 120.7 \mu\text{A/V} \quad r_o = 2.2 \text{M}\Omega$$

ResPrB.I-15

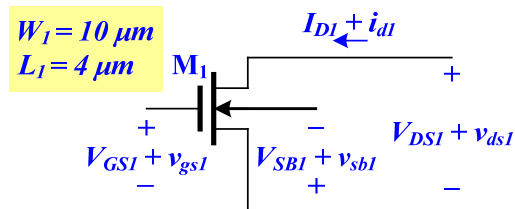Problema 3(c)

- $V_{TN} = V_{TNO} + \gamma_n \left(\sqrt{2\Phi_F + V_{SB}} - \sqrt{2\Phi_F} \right) = 1.123 \text{ V}$

$$M_1 \equiv \text{SAT} : V_{GS1} - V_{TN} = 0.877 \text{ V} < V_{DS1} = 3 \text{ V}$$



$$V_{SB1} = 1.5 \text{ V} \quad V_{GS1} = 2 \text{ V} \quad V_{DS1} = 3 \text{ V}$$

$$I_{D1} = \frac{1}{2} \frac{W_1}{L_1} K'_n (V_{GS1} - V_{TN})^2 (1 + \lambda_n V_{DS}) = 108.9 \mu\text{A}$$

ResPrB.I-16

Problema 3(c)

- Modelo pequeña señal:

$$g_m = \sqrt{2 \frac{W}{L} K'_n I_{D1} (1 + \lambda_n V_{DS1})} = 248.4 \mu\text{A/V}$$


$$g_{mb} = \frac{\gamma_n g_m}{2\sqrt{2\Phi_F + V_{SB}}} = 41.87 \mu\text{A/V}$$

$$g_{ds} = \frac{\lambda_n I_{D1}}{(1 + \lambda_n V_{DS1})} = 0.43 \mu\text{A/V}, \quad r_{ds} = g_{ds}^{-1} = 2.32 \text{M}\Omega$$

ResPrB.I-17

Problema 3(c)

- Circuito equivalente de pequeña señal:

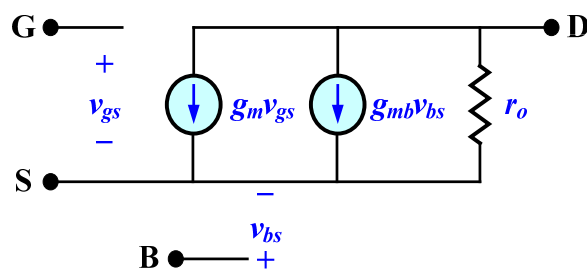


$$g_m = 248.4 \mu\text{A/V} \quad g_{mb} = 41.87 \mu\text{A/V} \quad r_o = 2.32 \text{M}\Omega$$

ResPrB.I-18

Problema 3(d)

- $V_{TN} = V_{TP} - \gamma_p \left(\sqrt{2|\Phi_F| - V_{SB}} - \sqrt{2|\Phi_F|} \right) = -1.273 \text{ V}$
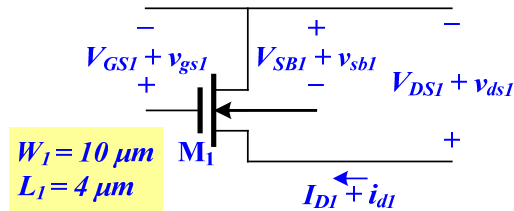
$$M_1 \equiv SAT : V_{GS1} - V_{TP} = -0.727 \text{ V} > V_{DS1} = -3 \text{ V}$$



$$V_{SBI} = -1.5 \text{ V} \quad V_{GS1} = -2 \text{ V} \quad V_{DS1} = -3 \text{ V}$$

$$I_{D1} = -\frac{1}{2} \frac{W_1}{L_1} K'_p (V_{GS1} - V_{TP})^2 (1 - \lambda_p V_{DS}) = -29 \mu\text{A}$$

ResPrB.I-19

Problema 3(d)

- Modelo pequeña señal:

$$g_m = \sqrt{2 \frac{W}{L} K'_p |I_{D1}| (1 - \lambda_p V_{DS1})} = 79.7 \mu\text{A/V}$$


$$g_{mb} = \frac{\gamma_p g_m}{2\sqrt{2|\Phi_F| - V_{SB}}} = 15.7 \mu\text{A/V}$$

$$g_{ds} = \frac{\lambda_p |I_{D1}|}{(1 - \lambda_p V_{DS1})} = 0.2 \mu\text{A/V}, \quad r_{ds} = g_{ds}^{-1} = 5 \text{ M}\Omega$$

ResPrB.I-20

Problema 3(d)

- Circuito equivalente de pequeña señal:

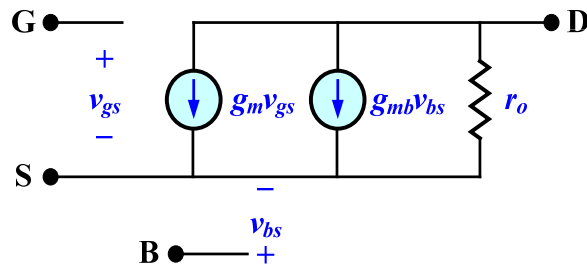


$$g_m = 79.7 \mu\text{A/V} \quad g_{mb} = 15.7 \mu\text{A/V} \quad r_o = 5 \text{M}\Omega$$

ResPrB.I-21

Problema 4(a)

- Parámetros de geometría:

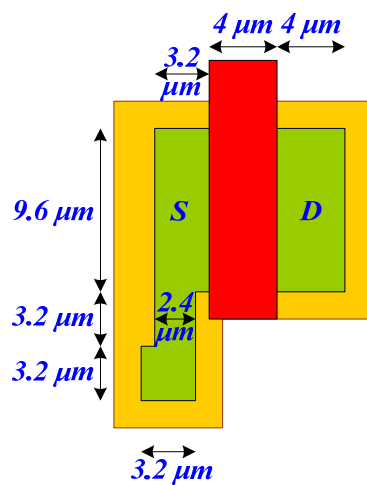

$$W = 9.6 \mu\text{m}$$

$$L = 4 \mu\text{m}$$

$$A_S = 48.64 \mu\text{m}^2$$

$$P_S = 40 \mu\text{m}$$

$$A_D = 38.4 \mu\text{m}^2$$

$$P_D = 27.2 \mu\text{m}$$

ResPrB.I-22

Problema 4(a)

- Capacidades de puerta (M saturado):

$$C_{gs} = \frac{2}{3}WLC_{ox} + WC_{gso} = 46.2 \text{ fF}$$

$$C_{gd} = WC_{gdo} = 1.92 \text{ fF}$$

$$C_{gb} = LC_{gbo} = 0.4 \text{ fF}$$

- Capacidades de drenador y fuente:


$$C_{db} = \frac{C_j A_D}{(1 + (V_{DB}/\phi_B))^{m_j}} + \frac{C_{jsw} P_D}{(1 + (V_{DB}/\phi_B))^{m_{jsw}}} = 10 \text{ fF}$$

$$C_{sb} = \frac{C_j A_S}{(1 + (V_{SB}/\phi_B))^{m_j}} + \frac{C_{jsw} P_S}{(1 + (V_{SB}/\phi_B))^{m_{jsw}}} = 20 \text{ fF}$$

ResPrB.I-23

Problema 4(b)

- Parámetros de geometría:

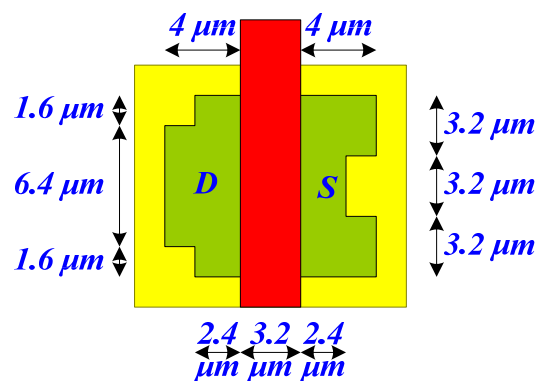

$$W = 9.6 \mu\text{m}$$

$$L = 3.2 \mu\text{m}$$

$$A_S = 33.28 \mu\text{m}^2$$

$$P_S = 30.4 \mu\text{m}$$

$$A_D = 33.28 \mu\text{m}^2$$

$$P_D = 27.2 \mu\text{m}$$

ResPrB.I-24

Problema 4(b)

- Capacidades de puerta (M saturado):

$$C_{gs} = \frac{2}{3}WLC_{ox} + WC_{gso} = 37.35 \text{ fF}$$

$$C_{gd} = WC_{gdo} = 1.92 \text{ fF} \quad C_{gb} = LC_{gbo} = 0.32 \text{ fF}$$

- Capacidades de drenador y fuente:

$$C_{db} = \frac{C_j A_D}{\left(1 + (|V_{DB}/\phi_B|)\right)^{m_j}} + \frac{C_{jsw} P_D}{\left(1 + (|V_{DB}/\phi_B|)\right)^{m_{jsw}}} = 9.156 \text{ fF}$$

$$C_{sb} = \frac{C_j A_S}{\left(1 + (|V_{SB}/\phi_B|)\right)^{m_j}} + \frac{C_{jsw} P_S}{\left(1 + (|V_{SB}/\phi_B|)\right)^{m_{jsw}}} = 14.187 \text{ fF}$$

ResPrB.I-25